

ECE570 Lecture 16: Diagnosis


Jeffrey Mark Siskind

School of Electrical and Computer Engineering


Fall 2013



A Circuit

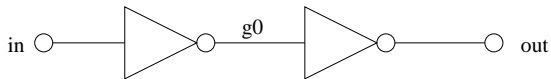

Another Circuit

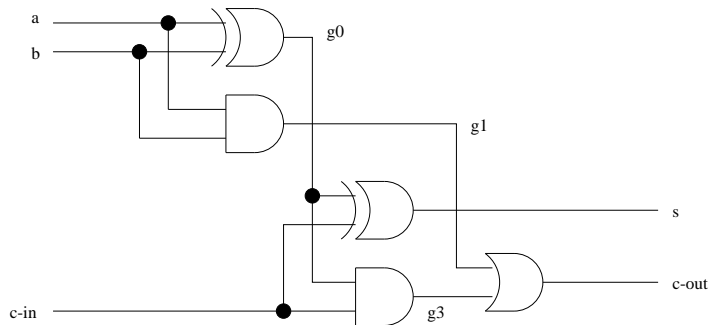

No Fault Model

“Transistors can fall from the sky”

A faulty component of n inputs can behave like *any* Boolean function of n inputs

Component Models—No Fault Model

$$\text{INVERT}(ab, x, out) \stackrel{\Delta}{=} \neg ab \rightarrow (out \leftrightarrow \neg x)$$

$$\text{AND}(ab, x, y, out) \stackrel{\Delta}{=} \neg ab \rightarrow (out \leftrightarrow (x \wedge y))$$

$$\text{OR}(ab, x, y, out) \stackrel{\Delta}{=} \neg ab \rightarrow (out \leftrightarrow (x \vee y))$$

$$\text{XOR}(ab, x, y, out) \stackrel{\Delta}{=} \neg ab \rightarrow (out \leftrightarrow \neg(x \leftrightarrow y))$$

Component Models—Stuck-At-Zero Fault Model

$$\text{INVERT}(ab, x, out) \triangleq [\neg ab \rightarrow (out \leftrightarrow \neg x)] \wedge [ab \rightarrow \neg out]$$

$$\text{AND}(ab, x, y, out) \triangleq [\neg ab \rightarrow (out \leftrightarrow (x \wedge y))] \wedge [ab \rightarrow \neg out]$$

$$\text{OR}(ab, x, y, out) \triangleq [\neg ab \rightarrow (out \leftrightarrow (x \vee y))] \wedge [ab \rightarrow \neg out]$$

$$\text{XOR}(ab, x, y, out) \triangleq [\neg ab \rightarrow (out \leftrightarrow \neg(x \leftrightarrow y))] \wedge [ab \rightarrow \neg out]$$

Component Models in Scheme—I

```
(define (clauses p atomic-formulas)
  (all-values
    (let ((clause
           (map (lambda (atomic-formula)
                  (list (a-boolean) atomic-formula))
                 atomic-formulas)))
      (when (apply p (map first clause)) (fail))
      (map negate-literal clause))))
```

Component Models in Scheme—II

```
(define (clauses p atomic-formulas)
  (prime-implicates
   (all-values
    (let ((clause
          (map (lambda (atomic-formula)
                 (list (a-boolean) atomic-formula))
                 atomic-formulas)))
      (when (apply p (map first clause)) (fail))
      (map negate-literal clause))))))
```


Component Models in Scheme—III

```
(define (make-inverter fault-model ab x out)
  (clauses (lambda (ab x out)
            (case fault-model
              ((none) (implies (not ab) (eq? out (not x))))
              ((stuck-at-zero)
               (and (implies (not ab) (eq? out (not x)))
                    (implies ab (not out))))
              (else (panic "Unrecognized fault model"))))
    (list ab x out)))
```

Component Models in Scheme—IV

```
(define (make-and-gate fault-model ab x y out)
  (clauses (lambda (ab x y out)
            (case fault-model
              ((none) (implies (not ab) (eq? out (and x y))))
              ((stuck-at-zero)
               (and (implies (not ab) (eq? out (and x y)))
                    (implies ab (not out))))
              (else (panic "Unrecognized fault model"))))
    (list ab x y out)))
```


Component Models in Scheme—V

```
(define (make-or-gate fault-model ab x y out)
  (clauses (lambda (ab x y out)
            (case fault-model
              ((none) (implies (not ab) (eq? out (or x y))))
              ((stuck-at-zero)
               (and (implies (not ab) (eq? out (or x y)))
                    (implies ab (not out))))
              (else (panic "Unrecognized fault model")))))
  (list ab x y out)))
```

Component Models in Scheme—VI


```
(define (make-xor-gate fault-model ab x y out)
  (clauses (lambda (ab x y out)
    (case fault-model
      ((none) (implies (not ab) (eq? out (not (eq? x y)))))
      ((stuck-at-zero)
        (and (implies (not ab) (eq? out (not (eq? x y))))
              (implies ab (not out))))
      (else (panic "Unrecognized fault model"))))
    (list ab x y out)))
```

System Description—I

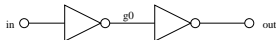

$$\text{INVERTER}(ab(g_0), in, g_0) \wedge \text{INVERTER}(ab(g_1), g_0, out)$$

System Description—II

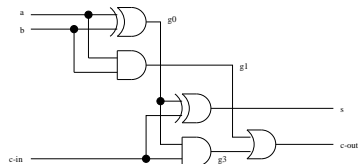


$$\begin{aligned} & \text{XOR}(ab(g_0), a, b, g_0) \wedge \\ & \text{AND}(ab(g_1), a, b, g_1) \wedge \\ & \text{XOR}(ab(g_2), g_0, c_{in}, s) \wedge \\ & \text{AND}(ab(g_3), g_0, c_{in}, g_3) \wedge \\ & \text{OR}(ab(g_4), g_3, c_{in}, c_{out}) \end{aligned}$$

System Description in Scheme—I



```
(define (make-double-inverter fault-model test-vector)
  (append (make-inverter fault-model '(ab g0) 'in 'g0)
    (make-inverter fault-model '(ab g1) 'g0 'out)
    test-vector))
```

System Description in Scheme—II

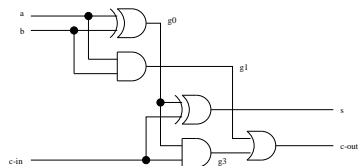

```
(define (make-full-adder fault-model test-vector)
  (append (make-xor-gate fault-model '(ab g0) 'a 'b 'g0)
    (make-and-gate fault-model '(ab g1) 'a 'b 'g1)
    (make-xor-gate fault-model '(ab g2) 'g0 'c-in 's)
    (make-and-gate fault-model '(ab g3) 'g0 'c-in 'g3)
    (make-or-gate fault-model '(ab g4) 'g3 'g1 'c-out)
    test-vector))
```


Four Classes of Atomic Formulas

AB formulas: $ab(g_0), ab(g_1), ab(g_2), ab(g_3), ab(g_4)$

inputs: a, b, c_{in}

outputs: s, c_{out}

internal nodes: g_0, g_1, g_3

Vectors—I

A *vector* is a CNF formula where each clause contains a single literal.

(A *vector* is also a DNF formula that contains a single minterm.)

An *input literal* is a true or negated input.

An *output literal* is a true or negated output.

An *AB literal* is a true or negated AB formula.

An *input vector* is a vector that contains only input literals.

An *output vector* is a vector that contains only output literals.

A *test vector* is a vector that contains only input or output literals.

A *diagnosis* is a vector that contains only AB literals.

Vectors—II

An input vector is a (partial) specification of the inputs to a circuit.

An output vector is a (partial) specification of the outputs of a circuit.

A diagnosis is a (partial) specification of which components are operational and which are faulty.

Diagnosis

Let Σ be a system description.

Let i be an input vector.

Let o be an output vector.

Let t be a test vector.

Let d be a diagnosis.

simulation Given Σ, i, d , find o such that $\Sigma \cup \{i, d\} \models o$

inverse simulation Given Σ, o, d , find i such that $\Sigma \cup \{o, d\} \models i$

diagnosis Given Σ, i, o , find d such that $\Sigma \cup \{i, o\} \models d$

Given Σ, t , find d such that $\Sigma \cup \{t\} \models d$

General Problem

Let Σ contain both the system description and some vectors.

Find a vector Φ that contains atomic formulas of a given class such that $\Sigma \models \Phi$ and that Φ is not covered by some other Ψ such that $\Sigma \models \Psi$.

General Algorithm

- 1 find the set Π all of the prime implicates of Σ
- 2 remove from Π any clause that contains atomic formulas that are not of the desired class
- 3 find all of the prime implicants of Π

Terminology

A *minimal conflict* is a prime implicate that contains only AB literals.

A *kernel diagnosis* is a prime implicant of the set of all minimal conflicts.